

Andrew Huynh
Student ID: 81586159

Pre-Lab 3: First-Order and Second-Order Circuits --- RC and RCL transient response

1. Calculations:

$$\text{Period} = 1/\text{frequency} = 1/100 \text{ kHz} = 1 \cdot 10^{-5} \text{ sec}$$

$$\text{Pulse width} = \text{Period}/2 = 1 \cdot 10^{-5}/2 = 5 \cdot 10^{-6} \text{ sec}$$


$$\tau \text{ (time constant)} = RC < 1/10 \text{ pulse width} \rightarrow R(1 \cdot 10^{-9} \text{ F}) < 1/10 (5 \cdot 10^{-6} \text{ sec})$$

Solving the previous inequality for R indicates that a total resistance of 500Ω is needed to obtain a time constant less than 1/10 of the pulse width. Therefore, the value of resistor R should be 450Ω .


2. Pspice

a)

$V_c(t)$ vs. time

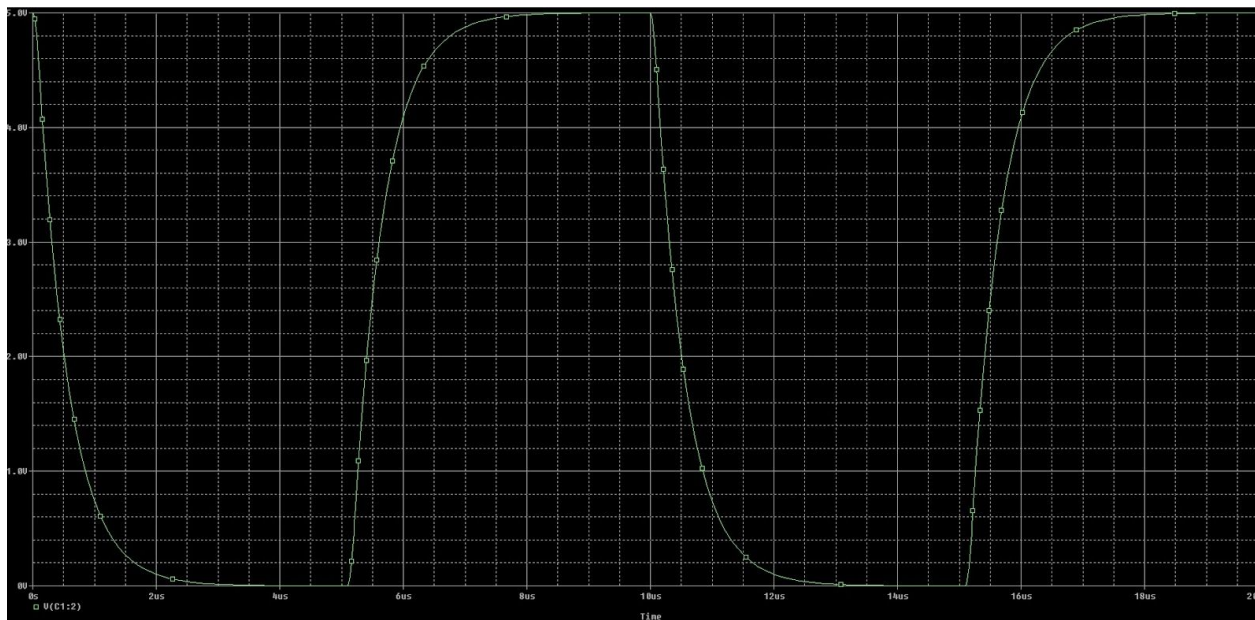

$i_c(t)$ vs. time

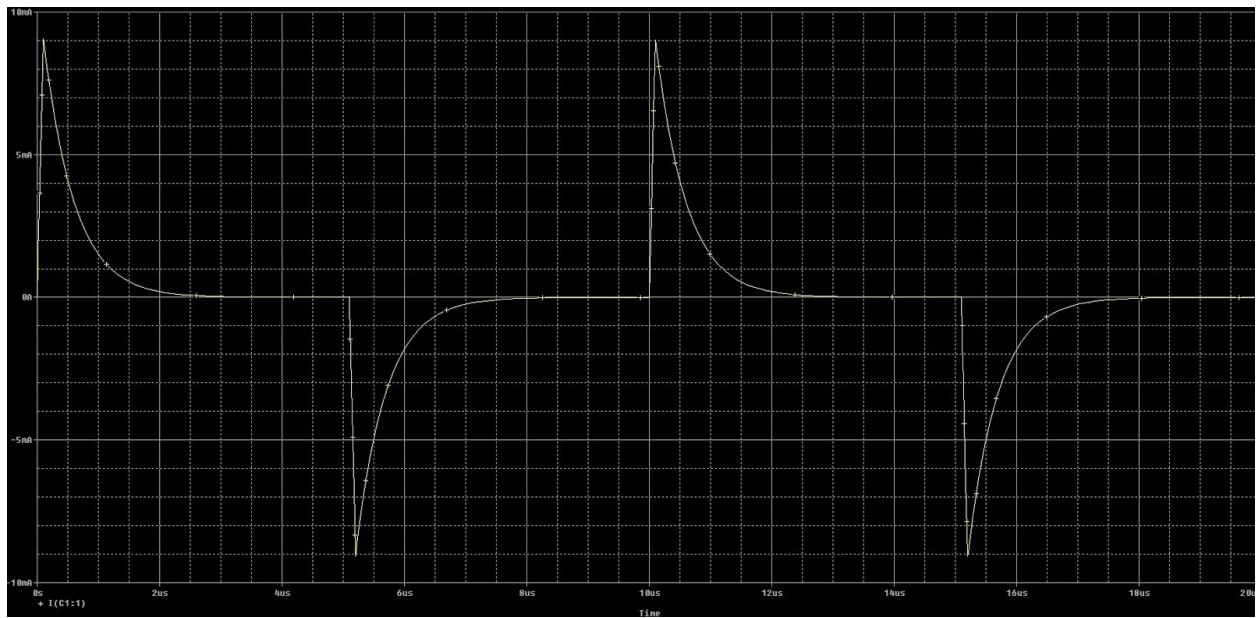

b) From the above waveform we can see that it takes approximately 5 microseconds for $V_c(t)$ to decrease from 5V to 1.84V (36.8% of the maximum voltage). This suggests that the time constant is about **5 micro sec**.

1. Calculations:

- a) For the circuit to be underdamped $R < 2\sqrt{L/C} \rightarrow R < 2\sqrt{10mH/1nF} \rightarrow R < 6325 \Omega$

Therefore the resistor must have a resistance of less than **6275 Ω** .

- b) For the circuit to be critically damped $R = 2\sqrt{L/C} \rightarrow R = 2\sqrt{10mH/1nF} \rightarrow R = 6325 \Omega$


Therefore the resistor must have a resistance of exactly **6275 Ω** .

- c) For the circuit to be overdamped $R > 2\sqrt{L/C} \rightarrow R > 2\sqrt{10mH/1nF} \rightarrow R > 6325 \Omega$


Therefore the resistor must have a resistance greater than **6275 Ω** .

2. Pspice

$V_c(t)$ vs. time (underdamped)

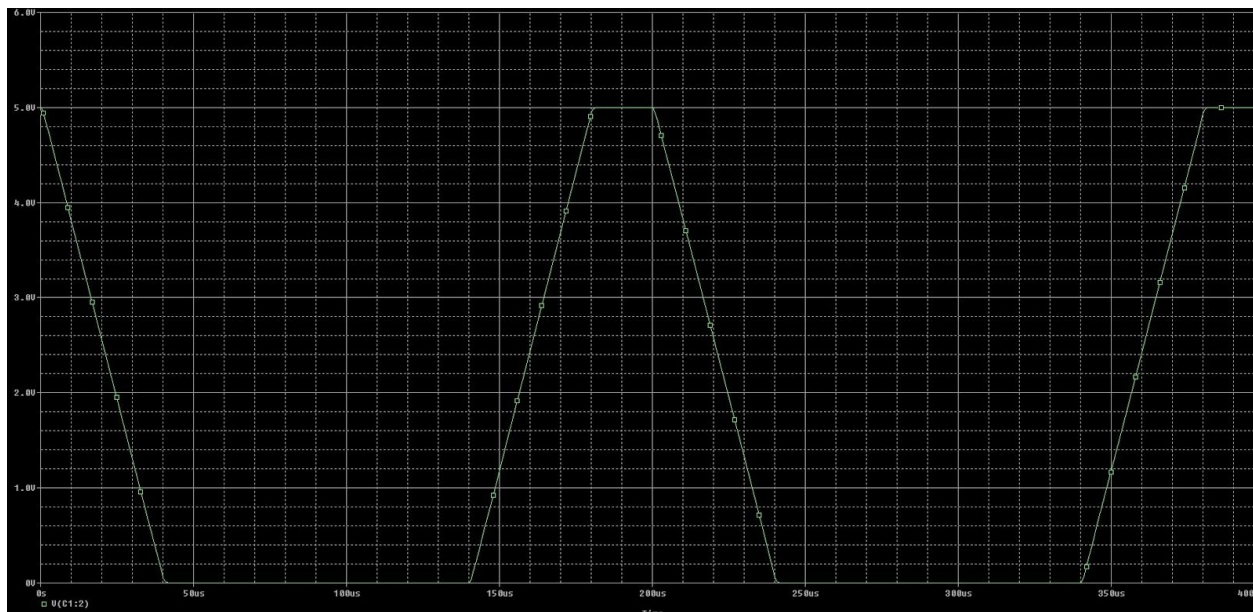

$V_c(t)$ vs. time (critically damped)

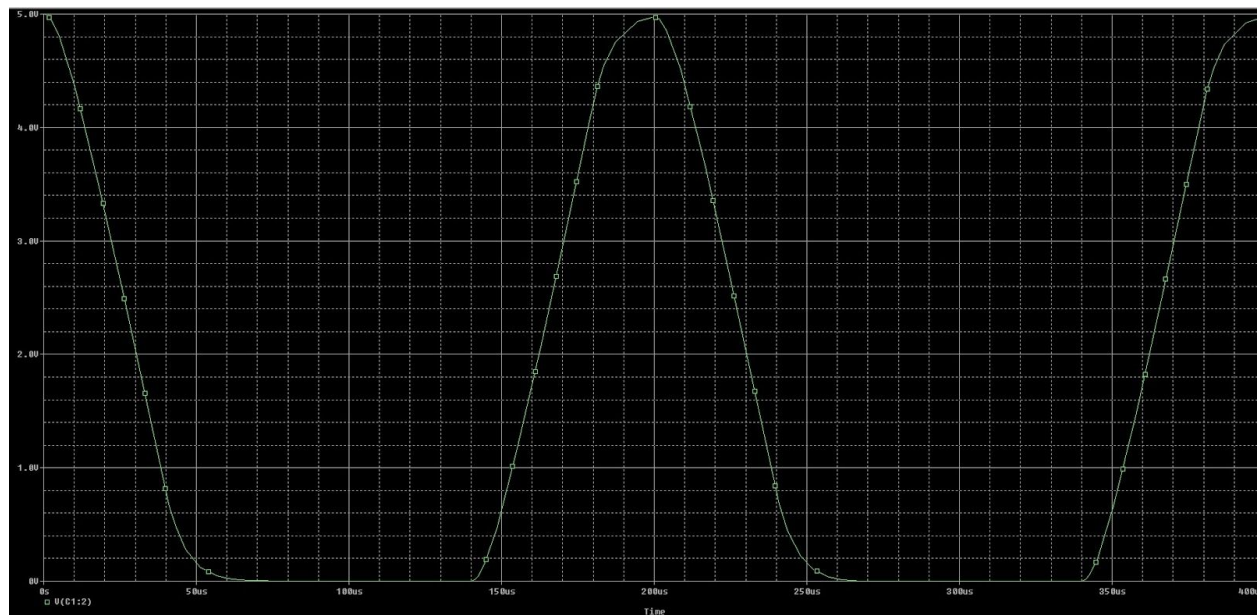

$V_c(t)$ vs. time (overdamped)

