

Thomas Dolan

ID #: 6662799


Mathematica HW 2

Due Friday Week 9 5pm

Consider charging an RC (for simplicity use $R = 1\text{k}\Omega$, $C = 1\text{pF}$) circuit with $V_s(t) = 5\text{ u}(t)$ (a step function). The capacitor is initially uncharged, i.e. $V_c(0) = 0\text{V}$. The analytic waveform for $V_c(t)$ is known to be $V_c(t) = 5(1 - e^{-t/(RC)})$ by solving the differential equation. We want to plot the waveform by estimating the time for V_c to rise from 0 to 1V, from 1 to 2V and so on until V_c reaches 5V **using the technique we discussed for CMOS inverter, i.e. estimating $\Delta\tau = \frac{\Delta Q_c}{I_c}$.**

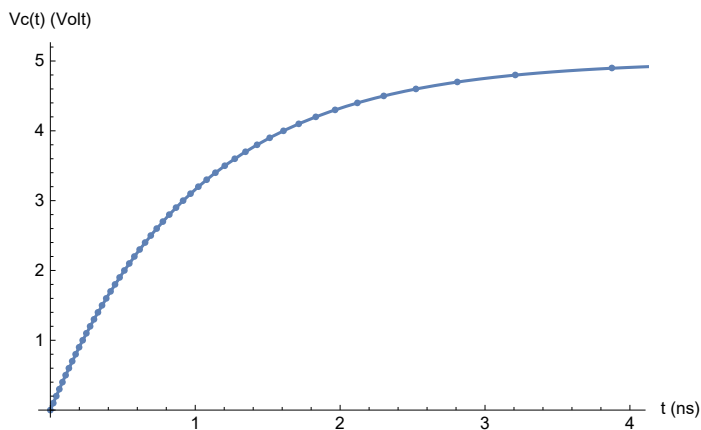- (a) Write a computer program (**Mathematica** or **otherwise, Matlab, Python, C++ etc.**) that will plot your estimated discrete waveform for $V_c(t)$ together with the analytic solution for $V_c(t)$.
- (b) If your program work for grids $\{0, 1, 2, 3, 4, 5\}$, repeat your calculation for finer grids of $\{0, 0.5, 1, 1.5, 2, 2.5, \dots\}$

Your result will look something like this. You should reproduce one similar to this with calculated value (dots) and analytical solution (continuous form) :



```

In[190]:= Clear["Global`*"]
c = 1;
r = 1;
ΔV = 0.5;
Vs = 5;
Vcrange = Range[0, 5, ΔV];
ic =  $\frac{Vs - Slot[1]}{r}$  & /@ Vcrange;
ic1 = Range[5, 0, -ΔV];
Avic = Table[ $\frac{ic[[i]] + ic[[i+1]]}{2}$ , {i, 1,  $\frac{Vs}{\Delta V}$ }] // N;
ΔQ = Table[c * ΔV, {i, 1,  $\frac{Vs}{\Delta V} + 1$ };
Δτ = Table[ $\frac{\Delta Q[[i]]}{Avic[[i]]}$ , {i, 1,  $\frac{Vs}{\Delta V}$ };
t = Table[Sum[Δτ[[i]], {j, i}], {i, 1,  $\frac{Vs}{\Delta V}$ };
t = Prepend[t, 0];
handc1 = Thread[{t, Vcrange}];
lp = ListPlot[handc1, Joined → True, Mesh → All, AxesLabel → {"time (ns)", "Vc (Volt)"}]
Plot[5 * (1 - (Exp[-x / (r * c)])), {x, 0, 20},
PlotRange → {{0, 20}, {0, 5}}, AxesLabel → {"time (ns)", "Vc (Volt)"}]

```

